


Exercise : 2.8

Problem Statement: after the following Boolean function, draw the corresponding logic circuit using derived gates, simplify the function and draw the logic circuits associated to all simplified forms of the initial function using only basic gates.


$$f_8(x, y, z) = x(\bar{y} \uparrow z) \vee \bar{x}(\bar{y} \oplus z) \vee y(x \oplus \bar{z})$$

Solution:

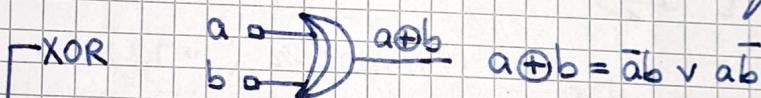
We'll start by defining the derived gates as their name, symbol and associated Boolean function :



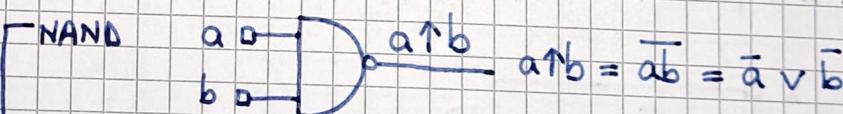
→ true when a-false and b-true, & a-true and b-false



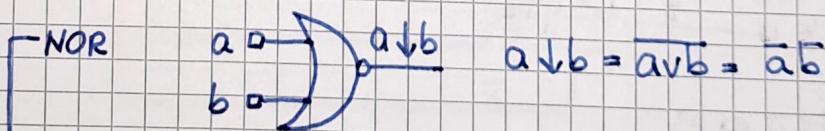→ true when a-false or b-false (negated and)



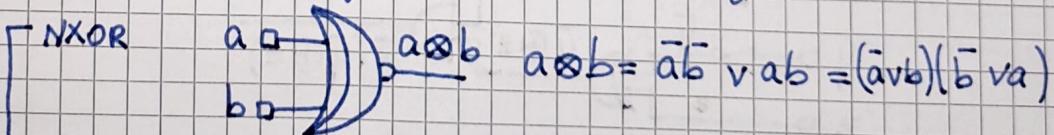→ true when a-false and b-false (negated or)




→ true when (a-false or b-true) and (b-false or a-true)
(negated XOR)


The next step is identifying the gates we need to use in order to represent $f \Rightarrow$

$$f_8(x, y, z) = x(\bar{y} \uparrow z) \vee \bar{x}(\bar{y} \oplus z) \vee y(x \oplus \bar{z})$$

↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓
 AND NAND OR NOR OR XOR NOT
 GATE GATE GATE GATE GATE GATE GATE


The basic gates and their symbols are:

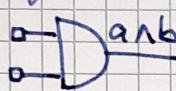AND  : conjunction ($a \wedge b$)

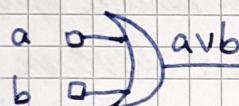
OR  : disjunction ($a \vee b$)

NOT  : negation ($\sim a$)


I. $x(\bar{y} \uparrow z)$:

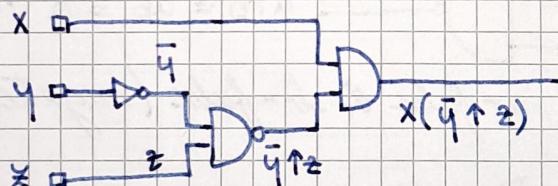


II. $\bar{x}(\bar{y} \oplus z)$

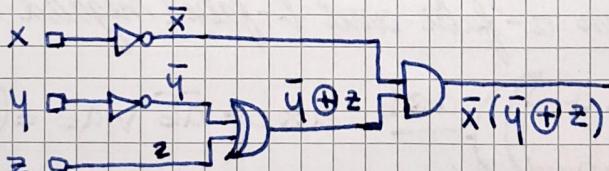

III. $y(x \oplus z)$

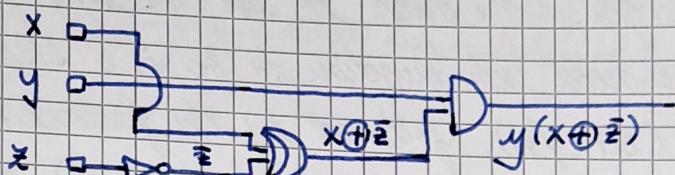

I, II, III =>

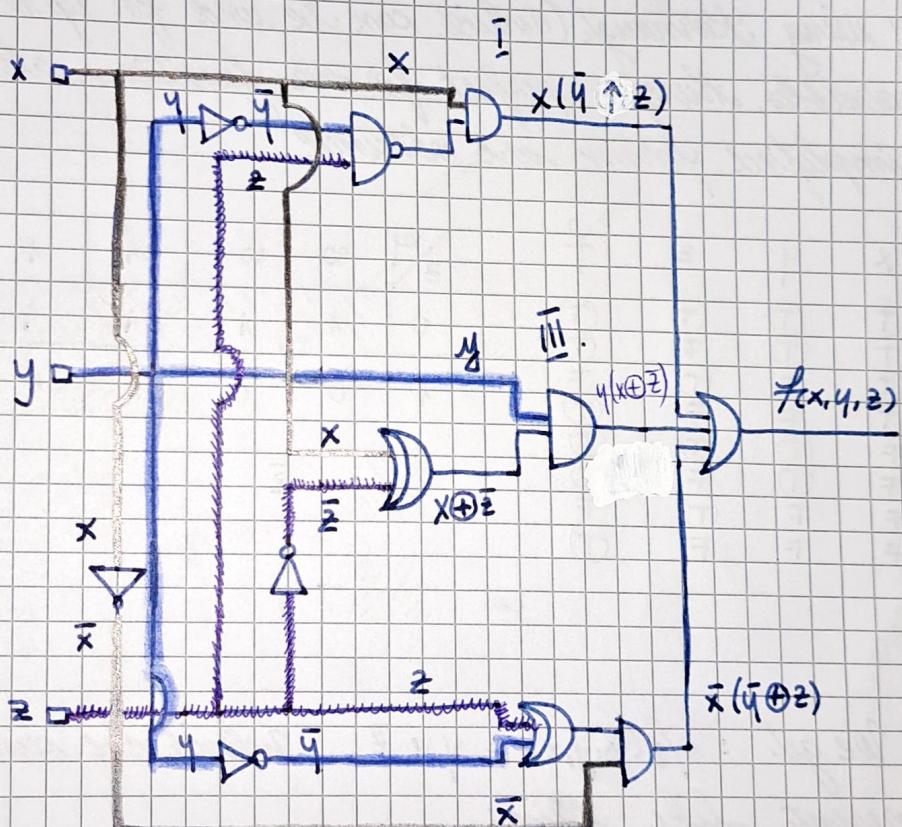

The next step is simplification: in order to use the simplification algorithm, we need our function to be in a disjunctive canonical form (DCF(f_0)), followed by the factorization process (the set of maximal monoms ($M(f_0)$), after which we select the central monoms ($C(f_0)$)). At last, by using Karnaugh (which can be used for up to 4 variables, therefore perfect for perfectly suited to our function), all simplified forms are obtained.

$$f(x, y, z) = x(\bar{y} \uparrow z) \vee \bar{x}(\bar{y} \oplus z) \vee y(x \oplus \bar{z}) \xrightarrow[\text{of } \uparrow]{\text{replacement}}$$

$$f(x, y, z) = x(\bar{y} \vee \bar{z}) \vee \bar{x}(\bar{y} \oplus z) \vee y(x \oplus \bar{z}) \Rightarrow$$

$$f(x, y, z) = x(y \vee \bar{z}) \vee \bar{x}(\bar{y} \oplus z) \vee y(x \oplus \bar{z}) \xrightarrow[\text{of } \oplus]{\text{replacement}}$$

$$f(x, y, z) = x(y \vee \bar{z}) \vee \bar{x}(yz \vee \bar{y}\bar{z}) \vee y(xz \vee \bar{x}\bar{z}) \xrightarrow[\text{distributivity}]{\text{using}}$$

$$f(x, y, z) = (xy \vee x\bar{z}) \vee (\bar{x}yz \vee \bar{x}\bar{y}\bar{z}) \vee (x\bar{y}z \vee \bar{x}y\bar{z}) \Rightarrow$$

$$f(x, y, z) = xy \vee x\bar{z} \vee \bar{x}yz \vee \bar{x}\bar{y}\bar{z} \vee x\bar{y}z \vee \bar{x}y\bar{z} \Rightarrow$$

$$f(x, y, z) = xy\bar{z} \vee xyz \vee x\bar{y}z \vee \bar{x}y\bar{z} \vee \bar{x}\bar{y}\bar{z} \vee x\bar{y}\bar{z} \Rightarrow$$

$$f(x, y, z) = xy\bar{z} \vee xyz \vee \bar{x}y\bar{z} \vee \bar{x}\bar{y}\bar{z} \vee \bar{x}\bar{y}\bar{z} \vee x\bar{y}\bar{z}$$

$$\max_1 = y$$

$$\max_2 = m_4 \vee m_5 \vee m_7 \vee m_6 = x$$

$$\max_3 = m_0 \vee m_1 \vee m_2 \vee m_3 = \bar{z}$$

$$\max_4$$

	$y\bar{z}$	00	01	11	10
x		m_0		m_3	m_2
	0	m_4	m_5	m_7	m_6
	1				

$M(f) = \{ \max_1, \max_2, \max_3 \} \rightarrow$ set of maximal monomies

$C(f) = \{ \max_1, \max_2, \max_3 \} \rightarrow$ set of central monomies

$$M(f) = C(f) \Rightarrow$$

$$\begin{aligned} f(x,y,z) &= \max_1 \vee \max_2 \vee \max_3 \\ &= y \vee x \vee \bar{z} \Rightarrow \\ &= x \vee y \vee \bar{z} \end{aligned}$$

The simplified function can be represented:

